

CSE635, Assignment 3, Main Memory, and Virtual Memory

Abdullah Aml

2101398

Contents

1-Bit Latch	1
Test Strategy	1
Test Output	1
Address Decoder 2	2
Test Strategy	2
Test Output	2
Mux	2
Test Strategy	2
Test Output	2
ALU	2
Test Strategy	2
Test output	3

1-Bit Latch

Test Strategy

D	Clk	q	qbar	comment
1	1	1	0	problem reacting to change in D
1	0	1	0	The latch does not hold D
0	1	0	1	Deasserting D (do latch depend on clk?)
1	0	0	1	output is not changing at the clock

Test Output

Time is now: 15 ns, D=1, clk=1, Actual q=1, Actual nq=0 Test PASSED
Time is now: 30 ns, D=1, clk=0, Actual q=1, Actual nq=0 Test PASSED
Time is now: 45 ns, D=0, clk=1, Actual q=0, Actual nq=1 Test PASSED
Time is now: 60 ns, D=1, clk=0, Actual q=0, Actual nq=1 Test PASSED

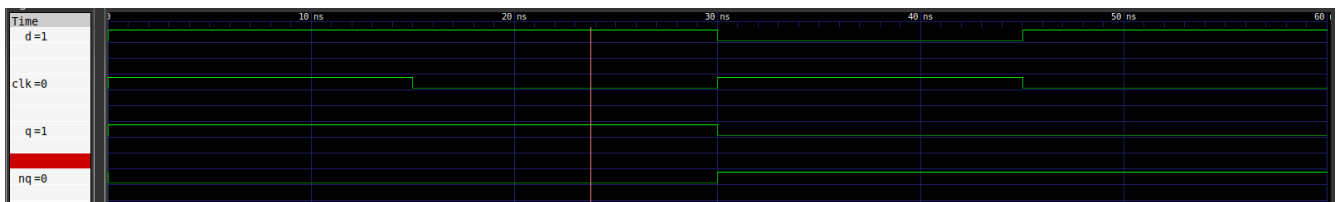


Figure 1: 1-bit Latch

Address Decoder 2

Test Strategy

address	decode	comment
7	10	Corner case for first case.
15	01	Corner case for second case (changing both bits).
17	01	does save the output(out side the range behaviour).
20	11	problem reacting to change in D.

Test Output

Time is now: 15 ns, address=7, decode=10, Actual decode=10 Test PASSED
Time is now: 30 ns, address=15, decode=01, Actual decode=01 Test PASSED
Time is now: 45 ns, address=17, decode=01, Actual decode=01 Test PASSED
Time is now: 60 ns, address=20, decode=11, Actual decode=11 Test PASSED

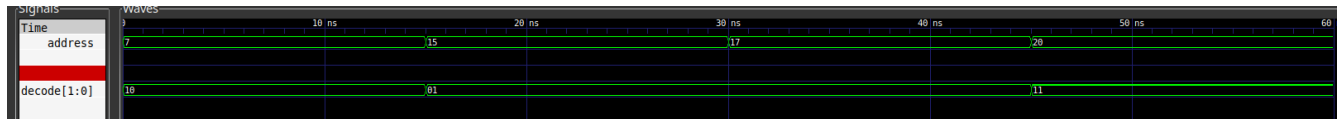


Figure 2: Address Decoder_2

Mux

Test Strategy

abcd	s	z	comment
0001	11	1	Not selecting the last input.
0001	00	0	stuck at 1 output.
1000	00	1	not selecting first input.
0010	10	1	Not selecting third input.
1000	01	0	stuck at 1 fault.
1100	01	1	Not selecting second input.

Test Output

Time is now: 15 ns, a,b,c,d=0001, s=11, z=1, Actual z=1 Test PASSED
Time is now: 30 ns, a,b,c,d=0001, s=00, z=0, Actual z=0 Test PASSED
Time is now: 45 ns, a,b,c,d=1000, s=00, z=1, Actual z=1 Test PASSED
Time is now: 60 ns, a,b,c,d=0010, s=10, z=1, Actual z=1 Test PASSED
Time is now: 75 ns, a,b,c,d=1000, s=01, z=0, Actual z=0 Test PASSED
Time is now: 90 ns, a,b,c,d=1100, s=01, z=1, Actual z=1 Test PASSED

ALU

Test Strategy

op	a	b	c	comment
01	1100	1101	1111	all ones test.
01	0011	1100	0111	maximum range(positive) of c.

op	a	b	c	comment
01	1111	0111	1000	maximum range (negative)of c.
01	0011	0011	0000	getting zero output.
00	1100	1101	1001	random test.
00	0011	1100	1111	all ones test of c.
00	1111	1001	1000	maximum range (negative)of c.
00	0011	0100	0111	maximum range(positive) of c.
00	0011	1101	0000	getting zero output.
10	0011	1111	1101	not changing op.
10	0111	0001	0111	max range(positive).
10	1100	0010	1000	max range(negative).
10	1101	1110	0110	not considering sign.
11	1101	1110	0000	not considering sign.
11	0111	0001	0111	max range(positive).
11	1000	0001	1000	max range(negative).
11	0111	1101	1110	random example.

Test output

```

time is now: 15 ns, op=sub, a=1100, b=1101, c=-1, actual c=1111 test passed
time is now: 30 ns, op=sub, a=0011, b=1100, c=7, actual c=0111 test passed
time is now: 45 ns, op=sub, a=1111, b=0111, c=-8, actual c=1000 test passed
time is now: 60 ns, op=sub, a=0011, b=0011, c=0, actual c=0000 test passed
time is now: 75 ns, op=add, a=1100, b=1101, c=-7, actual c=1001 test passed
time is now: 90 ns, op=add, a=0011, b=1100, c=-1, actual c=1111 test passed
time is now: 105 ns, op=add, a=1111, b=1001, c=-8, actual c=1000 test passed
time is now: 120 ns, op=add, a=0011, b=0100, c=7, actual c=0111 test passed
time is now: 135 ns, op=add, a=0011, b=1101, c=0, actual c=0000 test passed
time is now: 150 ns, op=mul, a=0011, b=1111, c=-3, actual c=1101 test passed
time is now: 165 ns, op=mul, a=0111, b=0001, c=7, actual c=0111 test passed
time is now: 180 ns, op=mul, a=1100, b=0010, c=-8, actual c=1000 test passed
time is now: 195 ns, op=mul, a=1101, b=1110, c=6, actual c=0110 test passed
time is now: 210 ns, op=div, a=1101, b=1110, c=1, actual c=0000 failed,
error messages: not considering sign.
time is now: 225 ns, op=div, a=0111, b=0001, c=7, actual c=0111 test passed
time is now: 240 ns, op=div, a=1000, b=0001, c=-8, actual c=1000 test passed
time is now: 255 ns, op=div, a=0111, b=1101, c=-2, actual c=1110 test passed

```

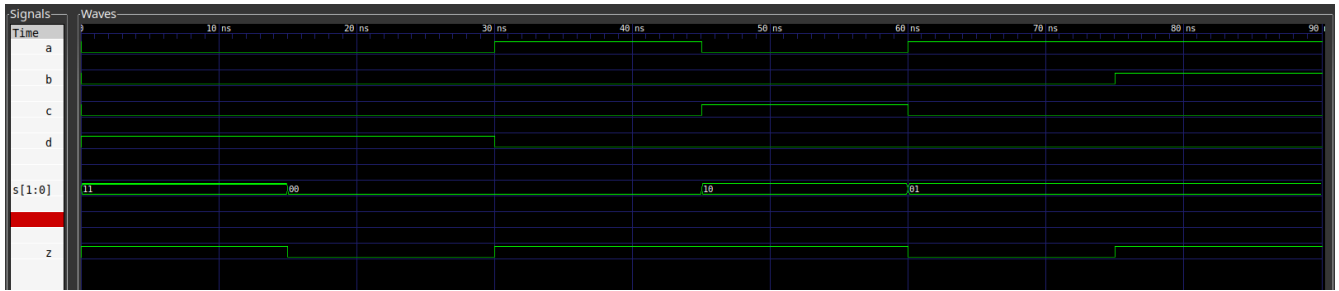


Figure 3: Mux simulation



Figure 4: ALU